

16-Steps Sequencer and Synthesizer

Zhuowen Lin & Jinyue Guo

11510818 & 11510478

Information Engineering, SUSTech

Speech Outline

- Inputs & Outputs
- Components of the circuit
- Result demonstration
- Further enhancements



Inputs & Outputs

Inputs

■ Switches

- ❑ Each of the 16 switches is assigned to a note at a specific time.
- ❑ When the time passes it, a note of the selected frequency will play.

■ Buttons

- ❑ BTNR: Save: assign any switch that is in the on position with the current frequency.
- ❑ BTNU: Switch frequency: rotate through the 16 frequencies.
- ❑ BTNC: Play/Pause
- ❑ BTNL: Reset: erase all assigned tones.

Outputs


- LEDs
 - LEDs above each switch.
 - Light up when a tone is playing on that particular switch.
- Seven Segment Display
 - Show which frequency is being worked with.
 - Rotate from 0 to F.
- Speaker
 - Sound wave at different frequencies.

Components of the Circuit

Button Toggle – Play & Pause

■ FSM

 - Toggle between two states exactly one time when the button is pressed



Button Debouncer

- Button bounce
 - Switch between states in FSM
- Debouncer
 - By Scott Larson of Digi-key
 - 10.5 ms stable input time

Clock Dividor – BPM setting

- Convert 100 MHz to lower frequencies
 - Used to set BPM

Counter – Tone / Switch Tracker

- Keep track of the tone
 - Speaker knows which tone to be played
 - Seven segment display knows which number to be displayed
- Keep track of the switch
 - Speaker knows which switch position to be played
 - Counter increasing speed: BPM
- T flip-flop
 - 4 bits \leftrightarrow 4 T flip-flops
 - Least significant bit: toggle each time
 - The other bits: toggle when all of bits below them are equal to one.

D Flip-Flop

- Remember the tone of 16 switches

Seven Segment Display

- Course Lab 3
 - Hexadecimal number


Square Wave Generator

- Change frequency dividing factor

Number	Tone	Max Count	Number	Tone	Max Count
0	0	0	8	d2	85131
1	a	227272	9	e2	75843
2	c1	191114	10	g2	63776
3	d1	170262	11	a2	56818
4	e1	150372	12	c3	47778
5	g1	127552	13	d3	42566
6	a1	113636	14	e3	37922
7	c2	95556	15	g3	31888

Sine Wave Generator

 - Waveform dictionary
 - 512-length arrays
 - Respective frequencies
- Value loader
 - Index: read value
 - Different max values



Sine Wave Generator - frequency

- Octave freq. divider
 - Save memory space
 - Use only Five distinct dictionaries
- Physical freq. divider
 - Divides oscillator clk into real sine wave clk

A ₄	440.00
A [#] ₄ /B ^b ₄	466.16
B ₄	493.88
C ₅	523.25
C [#] ₅ /D ^b ₅	554.37
D ₅	587.33
D [#] ₅ /E ^b ₅	622.25
E ₅	659.25
F ₅	698.46
F [#] ₅ /G ^b ₅	739.99
G ₅	783.99
G [#] ₅ /A ^b ₅	830.61
A ₅	880.00



Sine Wave Generator - Structure

- Waveform dictionary
- Physical freq. divider
- Pre-loader
 - Input tone (4bit)
 - Load dictionary
 - Maximum index
 - Octave div coefficient
- Octave freq. divider
- Output value loader
- Input:
 - Clk: std_logic
 - Tone: std_logic_vector (3 downto 0)
- Output:
 - Wave_out: std_logic_vector(7 downto 0)

Sine Wave Generator - Structure

- Why having two freq. dividers?
- Separate the waveform generating process
- Easier to create new dictionaries

Sine Wave Generator

  

PWM Encoder

- Nexys 4 DDR has a built-in PWM (Pulse Width Modulation) decoder, which is a low-pass filter.

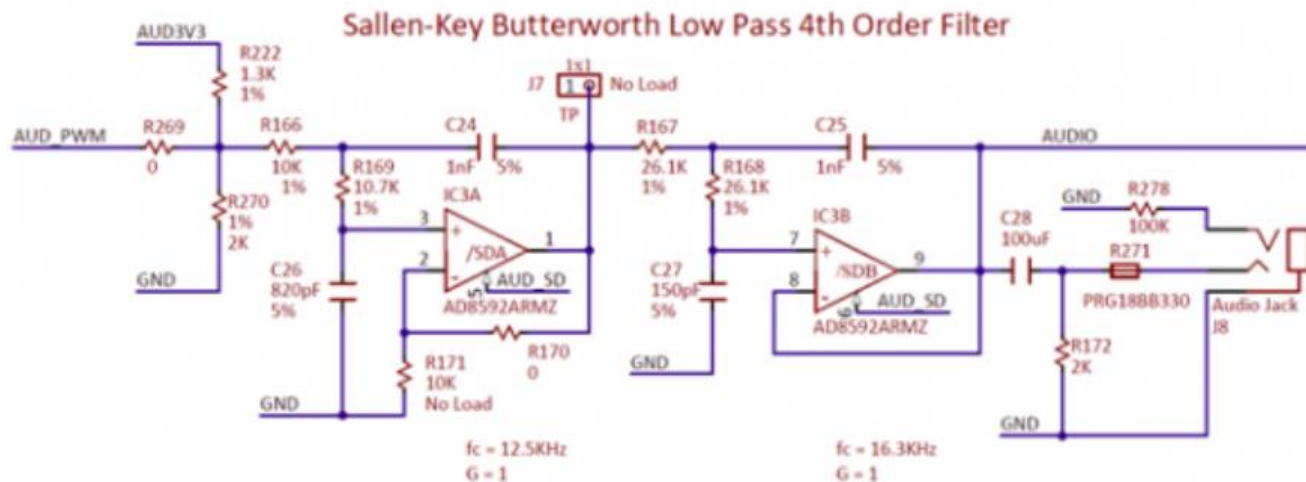


Figure 29. Sallen-Key Butterworth Low-Pass 4th Order Filter.

PWM Encoder

- Input: wave_in : std_logic_vector (7 downto 0)
- Calculate Duty Cycle threshold, according to PWM frequency
- Counter: smaller than threshold, output '1'; else '0'
- Output: std_logic



 
 


Figure 32. Representation of a PWM integrator producing an output voltage by integrating the pulse train.

PWM Encoder

 

Connecting Components

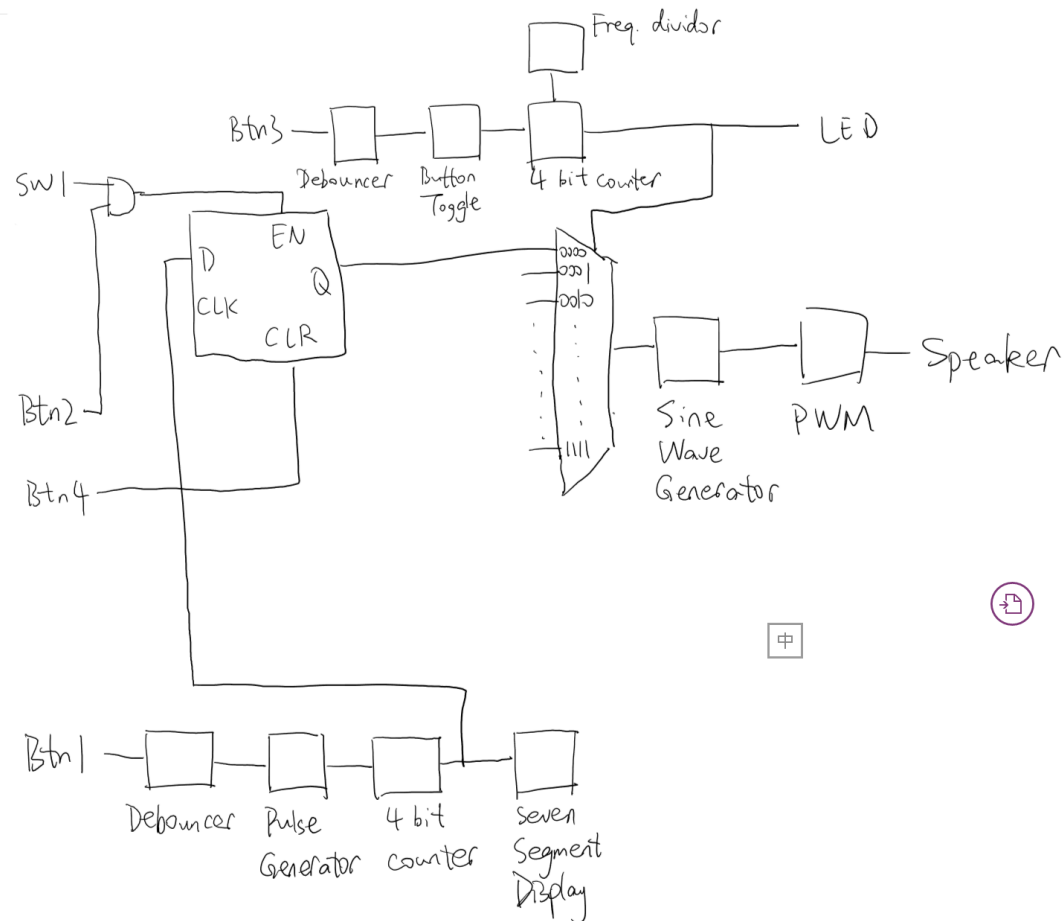

Result Demonstration

Further Development

- Better volume/ DA output solution
- Beats synthesizer
- Synchronization ports
- Selectable timbre (square, sine, toothsaw, etc.)
- Changeable BPM


Reference

- Frequencies for equal-tempered scale, A4 = 440 Hz
<http://pages.mtu.edu/~suits/notefreqs.html>
- Nexys 4 DDR Reference Manual
<https://reference.digilentinc.com/reference/programmable-logic/nexys-4-ddr/reference-manual>
- PWM Audio Tutorial using a FPGA
<https://www.youtube.com/watch?v=4byHVqXD-UI>
- Class Slides

Q&A

GitHub Page

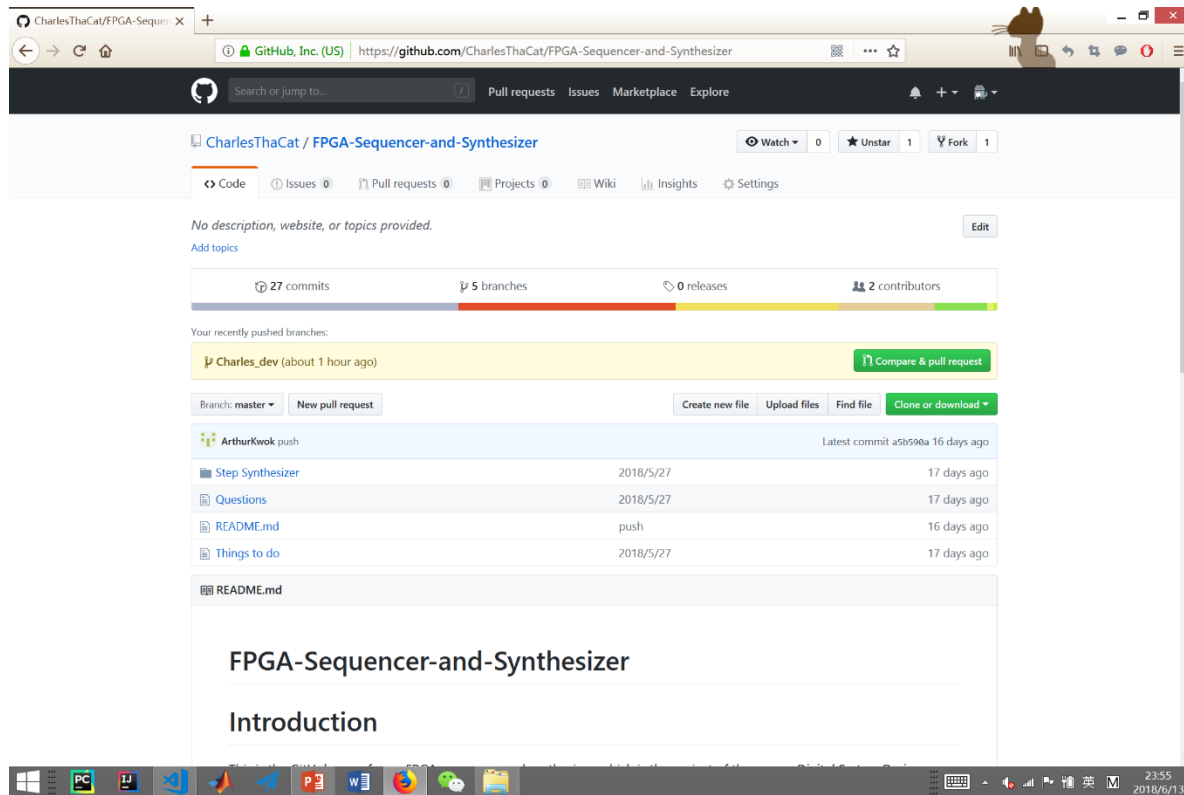- <https://github.com/CharlesThaCat/FPGA-Sequencer-and-Synthesizer>



Thank You!